

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING
BANGLADESH UNIVERSITY OF ENGINEERING & TECHNOLOGY
 COURSE NO.: EEE 208
 EXPT. NO. 02


Name of the Experiment: Study of BJT Biasing Circuits

Objective

To establish the proper operating point and to study the stability of the operating point with respect to changing β in different biasing circuits

Equipments

n-p-n transistor (C828,BC108)	one piece each
500k potentiometer	one piece
resistors	470 Ω 560 Ω 10K Ω
DC micrometer	0-100 μ A
multimeter	one unit
Trainer board	one unit

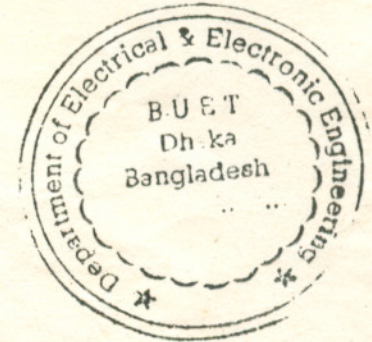

Circuit Diagrams

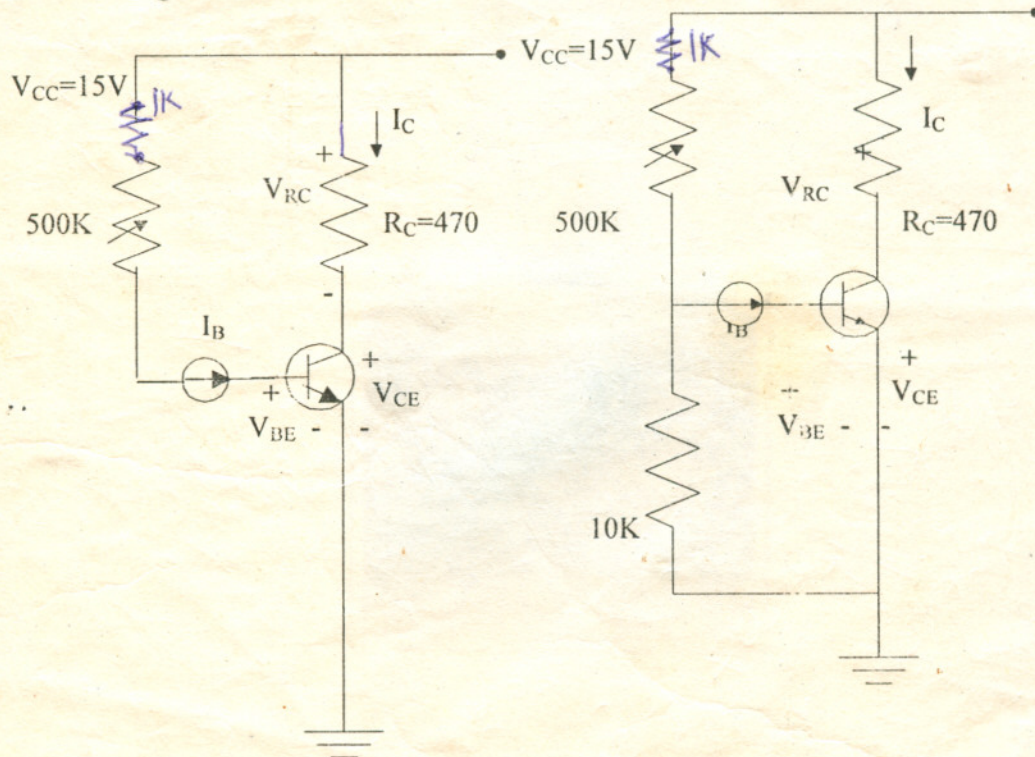


Fig. 1(a)

Fig. 1(b)

Fixed bias circuits

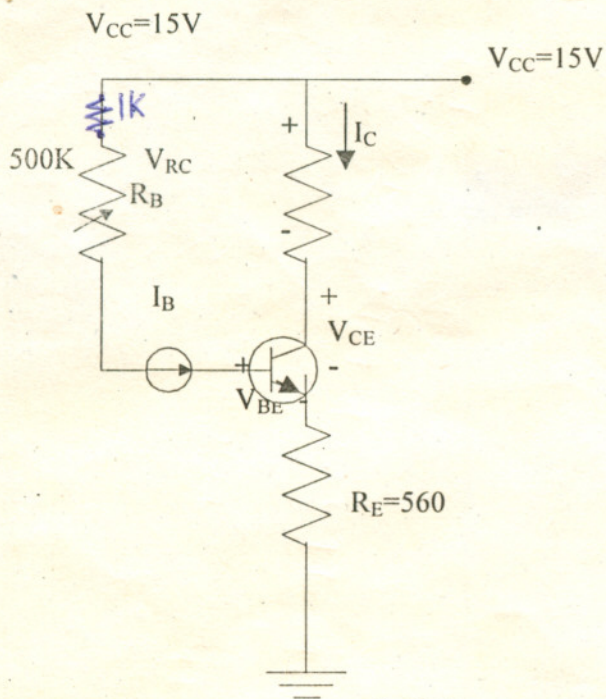


Fig. 2(a)

Self bias circuits


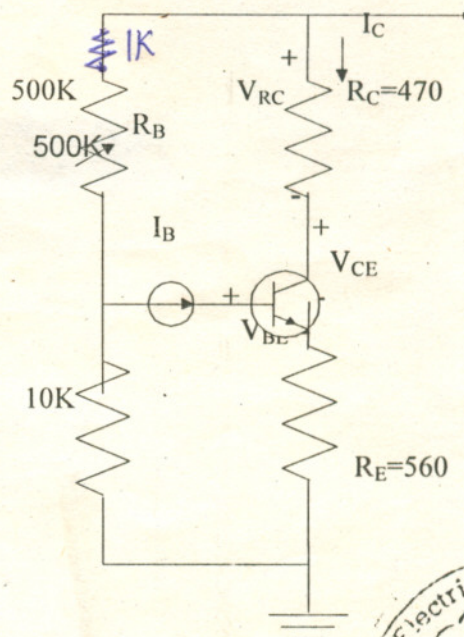


Fig. 2(b)

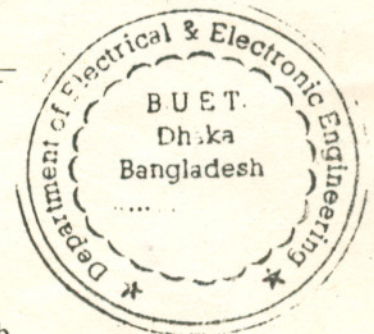

Prelab Work

Student must perform the following calculations before coming to the lab


1. For the circuit shown in Fig. 1(a) and 2(a), find expressions for I_{CQ} and V_{CQ} .

Procedures

1. Measure the value of R_c with multimeter and record.
2. Construct the fixed bias circuit with C828 transistors as shown in Fig. 1(a). Adjust 500K potentiometer until V_{CE} is approximately equal to $V_{CC}/2$. Measure V_{CE} , V_{BE} , V_{RC} and I_B . I_C can be calculated from V_{RC} and R_c .
3. Replace C828 by C829 keeping V_{CC} and 500K potentiometer fixed at values set in step 1. Measure V_{CE} , V_{BE} , V_{RC} and I_B .
4. Construct the fixed bias circuit with C828 transistors as shown in Fig. 1(b). Repeat step 2 and 3.
5. Construct the self bias circuit with C828 transistors as shown in Fig. 2(a). Repeat step 2 and 3.
6. Construct the self bias circuit with C828 transistors as shown in Fig. 2(b). Repeat step 2 and 3.

Reports

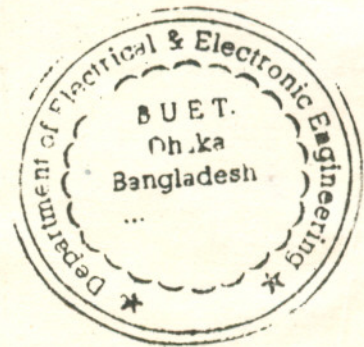1. Compare the circuits of Fig. 1(a) and 1(b) with respect to stability against variation in β and justify your answer.
2. Compare the circuits of Fig. 2(a) and 2(b) with respect to stability against variation in β and justify your answer.
3. Compare the stability of fixed bias circuits with that of self bias circuits.
4. Discuss the stability of fixed bias and self bias circuits against variation in temperature.
5. Determine β from the measured values of currents. Using this value for β and measured value of PB , calculate V_{CEQ} and I_{CQ} for prelab expressions. Compare had calculated values with experimental ones.



Updated by: Yeasir Arafat on 6th February, 2006