

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING
BANGLADESH UNIVERSITY OF ENGINEERING & TECHNOLOGY
COURSE NO.: EEE 208
EXPT. NO. 07

Name of the Experiment: Linear Application of Operational Amplifier

Objective

To investigate the use of operational amplifier as inverting multiplier, inverting summer, inverting integrator, inverting differentiator and differential amplifier.



Prelab Calculations and Simulation Using Spice (Home Work)

Students must perform the following SPICE simulations at home before attending the lab

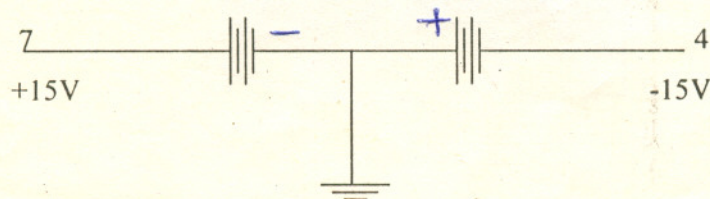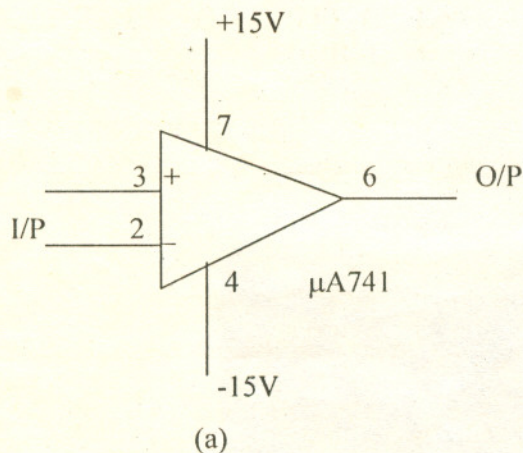1. For the different configurations shown in Fig (2), using SPICE, simulate the different configurations and sketch the simulated output waveforms.


Circuit Diagrams

N.B. The Op Amp $\mu A741$ has eight terminals to be connected as shown in Fig. (1).



(b) DC Supply Connection

Fig. (1)

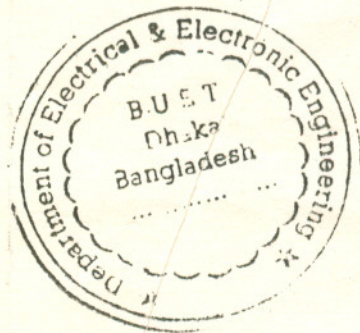

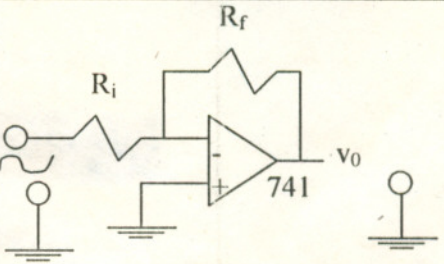
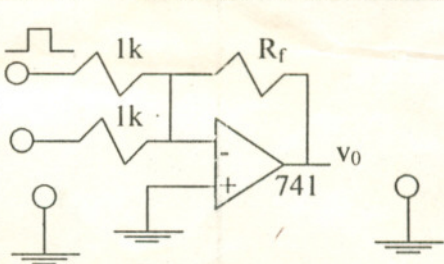
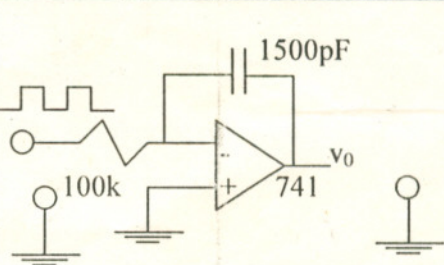
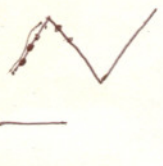
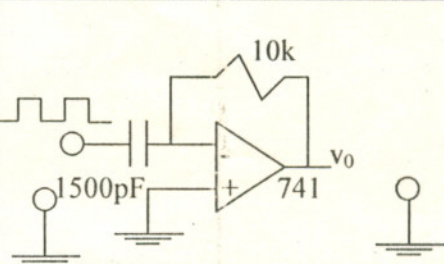
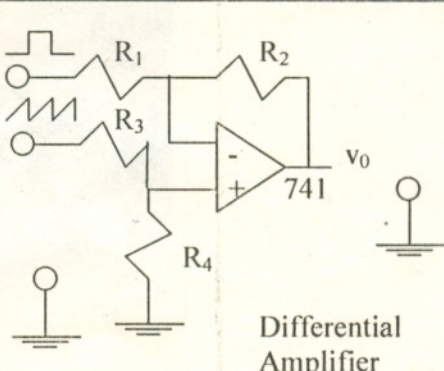
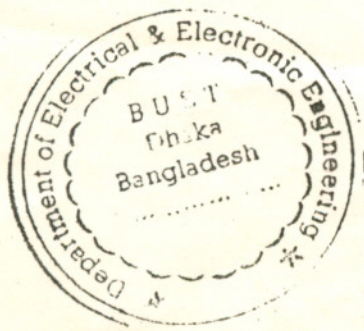
Operations	Circuits
<p>1. Inverting Multiplier $R_i=1k, R_f=1k, 10k, 100k$ $V_i=2v$ p-p sin, 1kHz</p>	
<p>2. Inverting Summer $R_f=1k, 10k, 100k$ $V_1=2v$ pp, 1kHz (rect or sin) $V_2=1v$ DC</p>	
<p>3. Inverting Integrator $V_i= 2v$ pp, 1kHz <i>or suitable</i></p>	
<p>4. Inverting Differentiator $V_i= 2v$ pp, 1kHz <i>or suitable</i></p> 	
<p>5. Differential Amplifier (as Subtractor) If $R_2/R_1 = R_4/R_3$(A) then $V_o = R_2/R_1(V_2 - V_1)$ $V_1 = 2v$ pp, 1kHz (sin or rect, to R_1) $V_2 = 1v$ DC, (to R_3) Satisfy (A) & set $R_2/R_1 = 1$ or 2</p>	 <p style="text-align: right;">Differential Amplifier</p>

Fig. 2




Procedures

1. Construct the circuits shown in Fig. (2). Apply the appropriate voltage in each case with frequencies of the order of 1 KHz. In each case measure the output waveform by the oscilloscope and sketch it in the Table 2

Table2: Linear Application Outputs.

Operations	Outputs		
	$R_f=1k$	$R_f=10k$	$R_f=100k$
1. Inverting Multiplier $R_i=1k, R_f=1k, 10k, 100k$ $V_i=2v$ p-p sin, 1kHz			
2. Inverting Summer $R_f=1k, 10k, 100k$ $V_1=2v$ pp, 1kHz(rect or sin) $V_2=1v$ DC			
3. Inverting Integrator $V_i=2v$ pp, 1kHz <u>or suitable</u>	Out put For $V_i=V_{sin}$	Out put For $V_i=V_{rec}$	Out put For $V_i=1V$
4. Inverting Differentiator $V_i=2v$ pp, 1kHz <u>or suitable</u>	Out put For $V_i=V_{sin}$	Out put For $V_i=V_{rec}$	
5. Differential Amplifier (as Subtractor) If $R_2/R_1 = R_4/R_3$ then.....(A) $V_o = R_2/R_1(V_2 - V_1)$ $V_1 = 2v$ pp, 1kHz (sin or rect, to R_1) $V_2 = 1v$ DC, (to R_3) Satisfy (A) & set $R_2/R_1=1$ or 2	$V_i=V_{sin}, R_2/R_1=1$	$V_i=V_{rec}, R_2/R_1=2$	

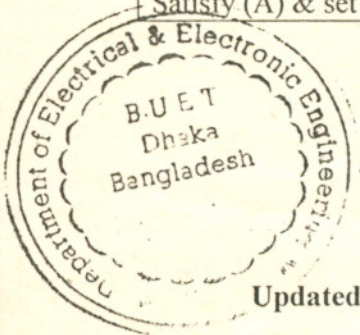

Reference: Op-amps & Linear ICs - Coughlin

Updated by: Yeasir Arafat on 7th February, 2006